

Diss. ETH No 13878

Single-Amplifier Biquadratic MOSFET-C Filters

A dissertation submitted to the
Swiss Federal Institute of Technology, Zürich
for the degree of
Doctor of Technical Sciences

presented by

Hanspeter Schmid

dipl. El.-Ing. ETH
born on February 8, 1969
citizen of Härkingen SO

accepted on the recommendation of
Prof. Dr. George S. Moschytz, examiner
Prof. Dr. Qiuting Huang, co-examiner

Hartung-Gorre Verlag, Konstanz, November 2000

Für Alexandra

Denn die Summe unseres Lebens
sind die Stunden, wo wir lieben

Contents

1	Introduction	1
1.1	Background	2
1.2	Analogue integrated filters	3
1.3	Outline of this dissertation	4
I	The System Level	7
2	The universal active element	9
2.1	Background	10
2.2	Introduction	11
2.3	Nullors and the universal active element	14
2.4	Operational amplifiers	17
2.5	Current conveyors	22
2.6	Implementation in CMOS	26
2.7	Conclusion	34
3	Current-mode and voltage-mode filters	37
3.1	Background	38
3.2	Current mode and voltage mode in the literature	39
3.3	Circuit transposition using signal-flow graphs	41
3.3.1	Introduction to circuit transposition	41
3.3.2	Driving-point signal-flow graphs	42
3.3.3	Transposition of signal-flow graphs	47
3.3.4	SFG and circuit transposition	50
3.4	Detailed comparisons	51
3.4.1	Ceteris paribus comparisons	51
3.4.2	Feedback and open-loop amplifiers	53
3.4.3	Mixed-signal circuits	58
3.5	Conclusion	59
4	Single-amplifier biquadratic filters (SABs)	61
4.1	Background	62
4.2	Introduction to SABs	62
4.2.1	Classification of SABs	62
4.2.2	Properties of Sallen-and-Key filters	65

4.3	Sensitivity	66
4.3.1	Introduction	66
4.3.2	Arbitrary-gain low-pass filter	67
4.3.3	Unity-gain low-pass filter	71
4.3.4	Application to integrated filters	74
4.3.5	Bandpass and high-pass filters	75
4.3.6	Appendix — proofs	75
4.4	Amplifier non-idealities	80
4.4.1	Current-mode Sallen-and-Key filters	80
4.4.2	Pole shifts	82
4.4.3	Parasitic zeros	83
4.4.4	Practical example	85
4.4.5	Appendix	87
4.5	Conclusion	88

II The Transistor Level 89

5	Second-order MOSFET–C networks 91
5.1	Background 92
5.2	Introduction to MOSFET–C filters 92
5.3	A note on transistor models 94
5.4	Second-order MOSFET–C networks 97
5.4.1	Choosing analogue ground 99
5.5	Charge-pumped MOSFET–C filters 101
5.5.1	Choosing the signal swing 101
5.5.2	A charge pump for MOSFET–C filters . 103
5.5.3	Clock feed-through 105
5.6	Various influences on the THD 108
5.6.1	Frequency dependence of the THD . . 109
5.6.2	Mismatch-induced distortion 109
5.6.3	Distortion caused by cascading biquads 110
5.6.4	Distortion caused by amplifier output capacitance 112
5.7	MOSFET-only filters 113
5.8	Distortion simulation and measurement 114
5.8.1	Harmonic distortion derived from DC characteristics 114
5.8.2	Comparison of the methods 117
5.8.3	Measurement method 119
5.9	Conclusion 122

6	Implementation of the current amplifier	123
6.1	Background	124
6.2	Current amplifier structures	124
6.3	Fixed-gain current amplifier	125
6.3.1	Operation principle	126
6.3.2	Noise analysis	128
6.3.3	Trade-offs	130
6.4	Variable-gain current amplifier	131
6.4.1	Core of a variable-gain current amplifier	131
6.4.2	Complete variable-gain amplifier	134
6.5	Conclusion	135
7	Description of test chips and measurements	137
7.1	Background	138
7.2	Measurement electronics	139
7.2.1	Input voltage generator	139
7.2.2	Output I–V converter	140
7.2.3	Measurement equipment	140
7.3	First test chip	141
7.3.1	V–I converter and signal inputs	141
7.3.2	Current amplifier	142
7.3.3	Pair of biquadratic filters	143
7.3.4	Variable-gain current-amplifier core . .	144
7.4	Second test chip	146
7.4.1	V–I converter and signal inputs	146
7.4.2	Charge-pumped biquad	147
7.4.3	8-MHz 7th-order biquad cascade	150
7.4.4	Variable-gain current amplifier	151
7.4.5	Biquad with tunable f_p and q_p	155
III	Conclusion	157
8	Comparisons and trade-offs	159
8.1	Background	160
8.2	Comparison by figure of merit	162
8.3	Trade-offs	164
8.3.1	Local feedback and pole-Q stability . .	164
8.3.2	Input resistance and output capacitance	164
8.3.3	Maximum pole frequency and pole-Q variance	165
8.3.4	Signal swing, THD, and SNR	165
8.3.5	Cascadability and pole-Q variance . . .	165

8.3.6	Charge-pump or not?	166
8.4	Conclusion	166
9	Ideas for future research	167
	Glossary	171
	Bibliography	173
	The author's biography	185